

# Digital Electronics

---

## Computer and Electronics Engineering

Roger Sash  
Herb Detloff  
Alisa Gilmore

# Digital Electronics

## Objectives:

The objectives of this module are to:

- Become familiar with basic electrical concepts
- Understand and use digital AND and OR logic functions
- Test circuits using circuit simulation software


To accomplish the objectives, we will give you a short overview of electrical and digital logic concepts. You will then work with a partner to build circuits described later in the handout using the Electronic Workbench simulation program. A variety of circuits are described; however, you may not have time to complete the simulation of all of them.

The simulation program we will be using is MultiSim 8 by Electronics Workbench. [www.electronicworkbench.com](http://www.electronicworkbench.com). It is a user-friendly program which a user can create and test circuits in a relatively short time. It has a variety of components listed in a series of menus. One of the initial difficulties is finding the component you want. The circuits we are going to build start on page 13.

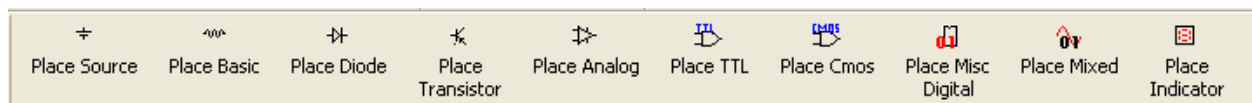
## How to Find Components

A list of component icons is shown along with the menu selections used to access them. The order of presentation is the same as the order in which you will be constructing the circuits.


If your menu toolbar only shows icons without the text which identifies them, you need to turn on the text so the toolbar is as shown below:




## How to turn on the Toolbar text

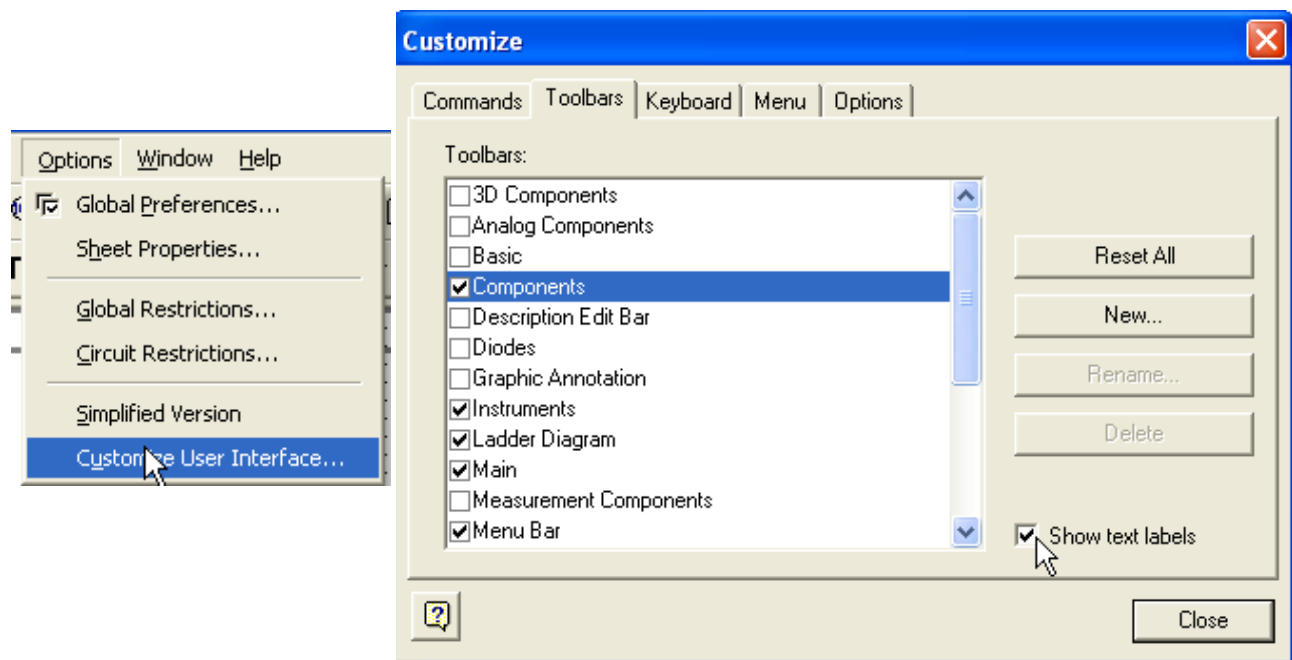

## Circuit 1:

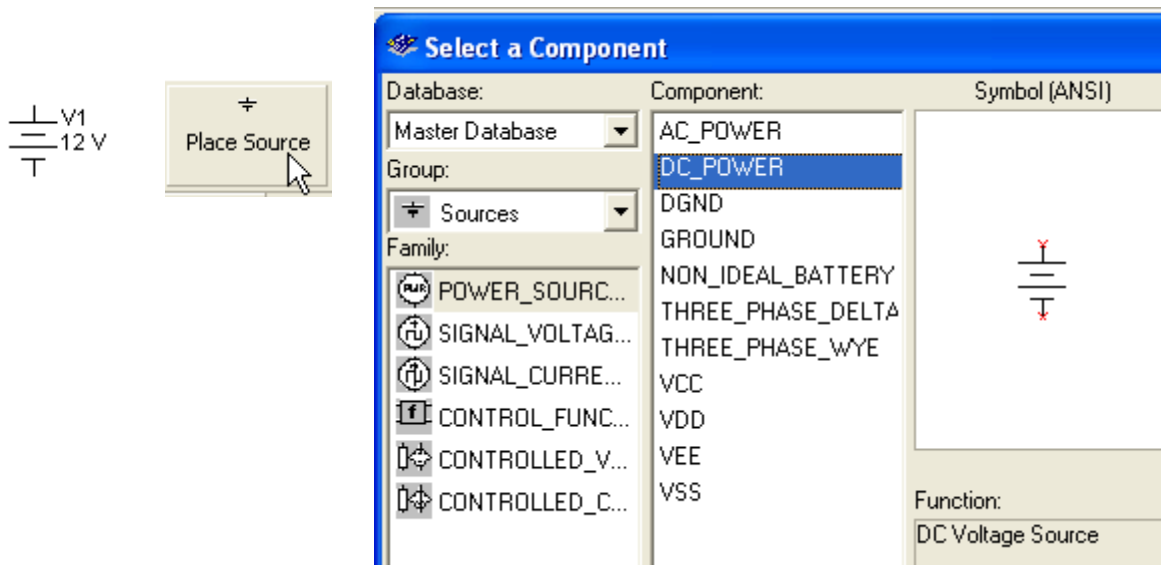

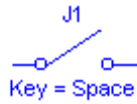

**Select a Component**

Database: Master Database

Component: CURRENT\_CONTROLLE

Symbol (ANSI)

Group: Basic


Family:

- RESISTOR\_S...
- RPACK
- POTENTIOME...
- CAPACITOR
- CAP\_ELECTR...
- CAPACITOR\_...
- CAP\_ELECTR...
- VARIABLE\_CA...
- INDUCTOR

Component List:

- DIPSW1
- DIPSW10
- DIPSW2
- DIPSW3
- DIPSW4
- DIPSW5
- DIPSW6
- DIPSW7
- DIPSW8
- DIPSW9
- PB\_DPST
- SPDT
- SPST
- TD\_SW1

Function: SPST Switch

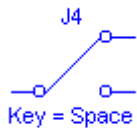

**Select a Component**

Database: Master Database

Component: CURRENT\_CONTROLLE

Symbol (ANSI)

Group: Basic

Family:

- BASIC\_VIRTU...
- RATED\_VIRT...
- 3D\_VIRTUAL
- RESISTOR
- RESISTOR\_S...
- RPACK
- POTENTIOME...
- CAPACITOR
- CAP\_ELECTR...
- CAPACITOR\_...
- CAP\_ELECTR...
- VARIABLE\_CA...
- INDUCTOR
- INDUCTOR\_S...
- VARIABLE\_IN...
- SWITCH
- TRANSFORM...
- NON\_LINEAR...


Component List:

- DIPSW1
- DIPSW10
- DIPSW2
- DIPSW3
- DIPSW4
- DIPSW5
- DIPSW6
- DIPSW7
- DIPSW8
- DIPSW9
- PB\_DPST
- SPDT
- SPST
- TD\_SW1
- VOLTAGE\_CONTROLLE


Function: SPDT Switch


Model Manuf. \ID: Generic\ILLUMINATED

Footprint Manuf. \Type: Generic\SPDT

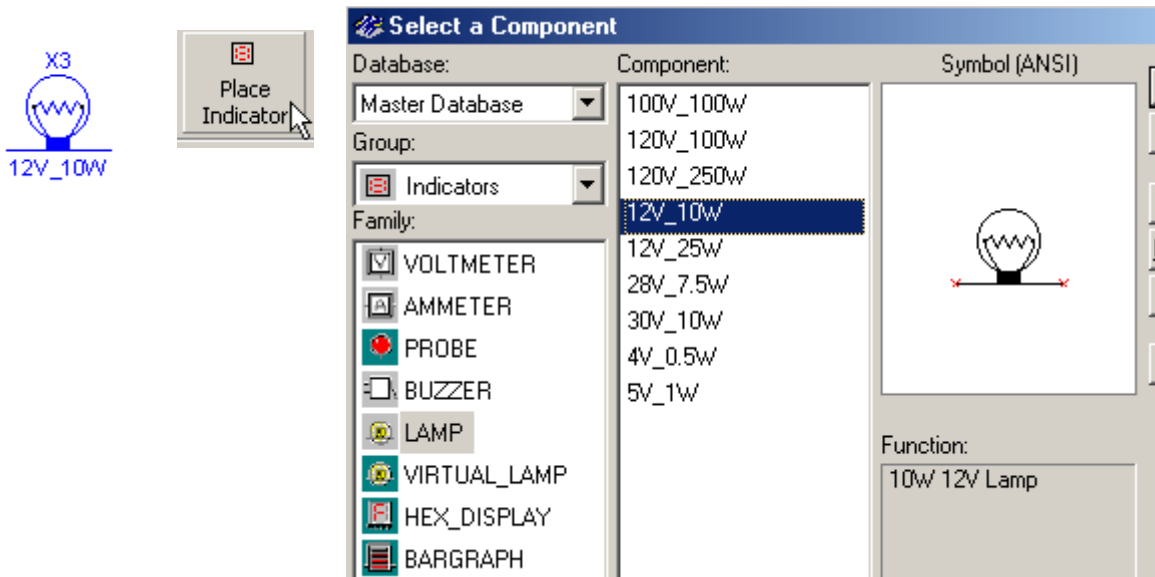

### Circuit 3:

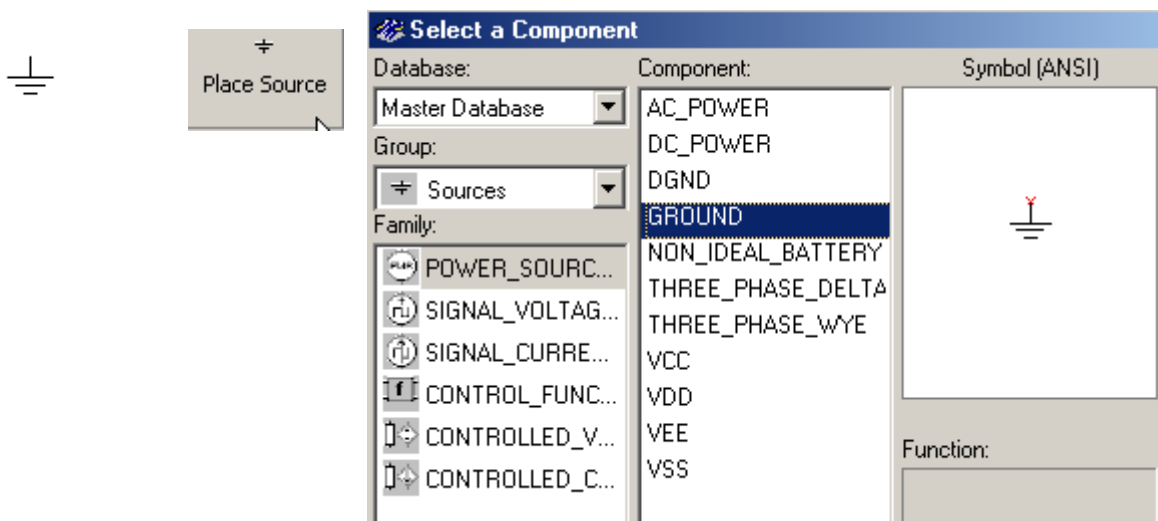

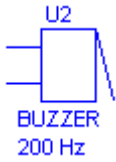

**Select a Component**

Database: Master Database

Component: BUZZER

Symbol (ANSI)


Group: Indicators

Family:

- VOLTMETER
- AMMETER
- PROBE
- BUZZER
- LAMP
- VIRTUAL\_LAMP
- HEX\_DISPLAY
- BARGRAPH

Function: Buzzer

Circuit 4:

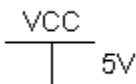

**Select a Component**

Database: Master Database


Component: VCC

Symbol (ANSI)

Group: Sources

Family:

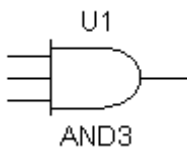- POWER\_SOURC...
- SIGNAL\_VOLTAG...
- SIGNAL\_CURRE...
- CONTROL FUNC...
- AC\_POWER
- DC\_POWER
- DGND
- GROUND
- NON\_IDEAL\_BATTERY
- THREE\_PHASE\_DELTA
- THREE\_PHASE\_WYE
- VCC
- VDD



**Select a Component**

Database: Master Database



Component: AND3

Symbol (ANSI)


Group: Misc Digital




Family:

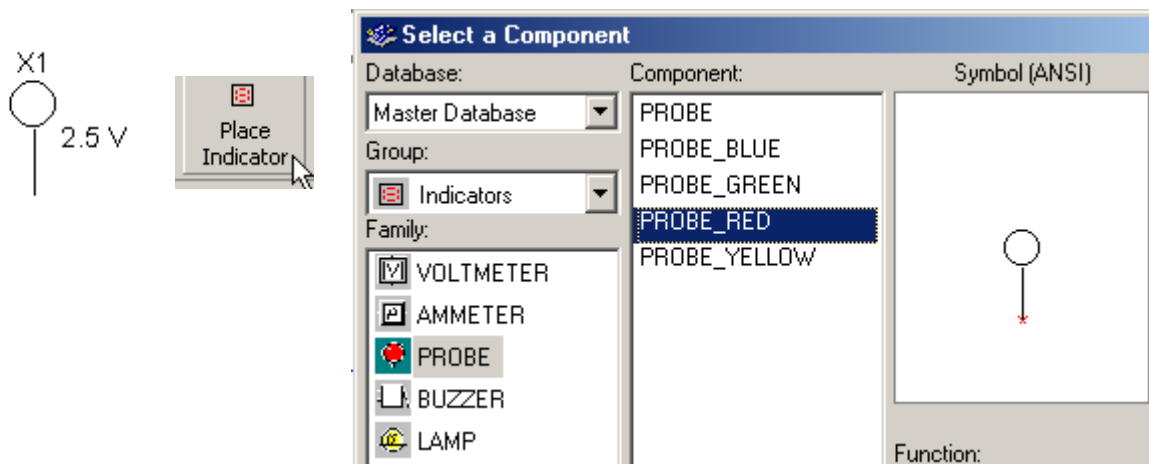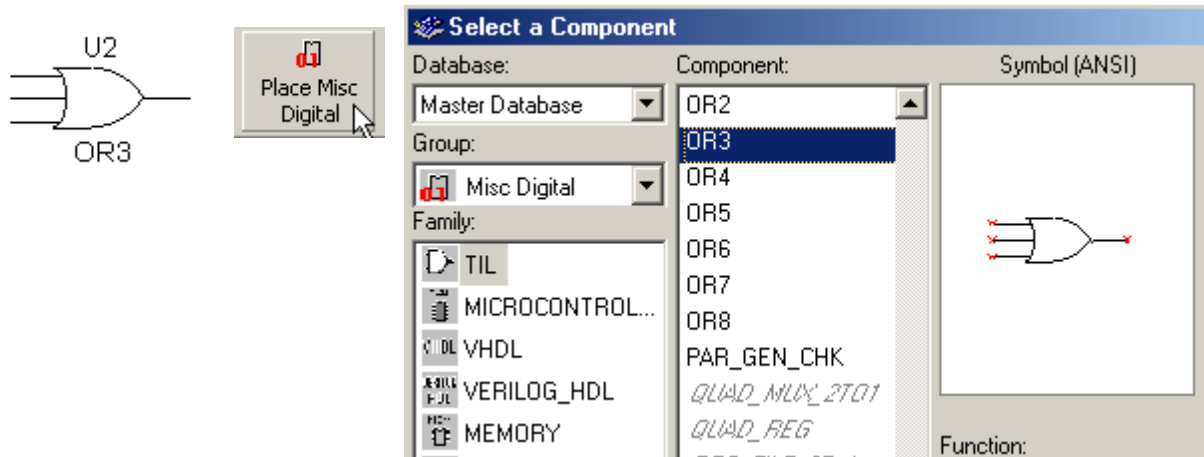- TIL
- MICROCONTROL...
- VHDL
- VERILOG\_HDL
- AND2
- AND3
- AND4
- AND5
- AND6
- AND7
- AND8
- BCD\_7SEG\_DCD
- BUFFER




### Circuit 5:

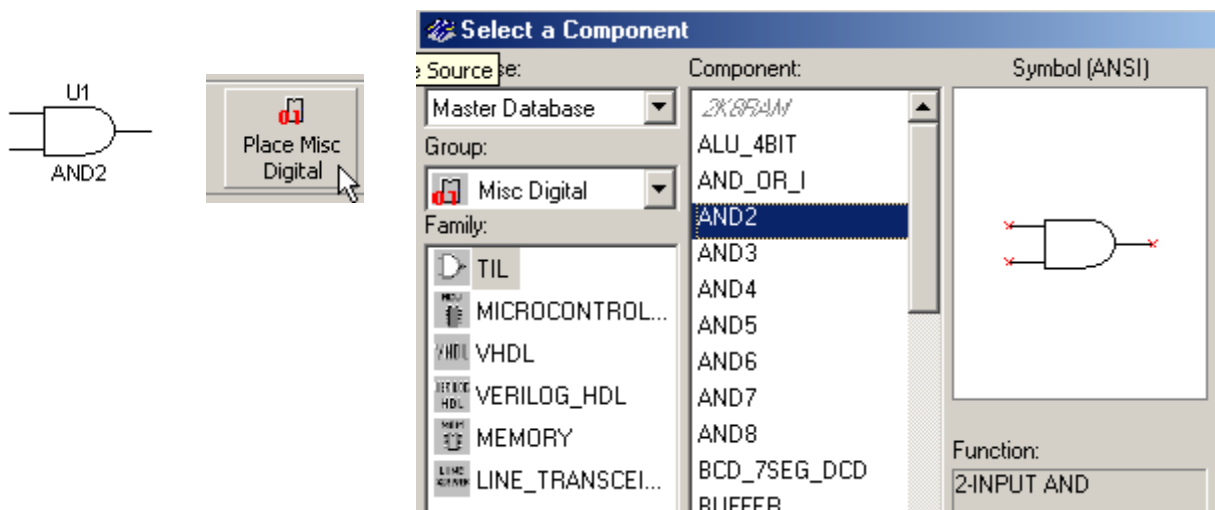

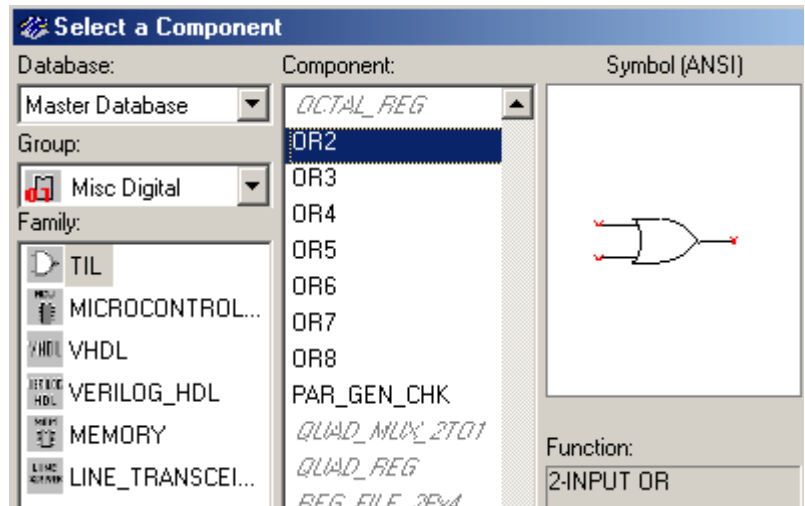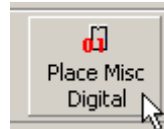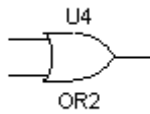


Double click the buzzer icon to change the buzzer to work with 5 volts.

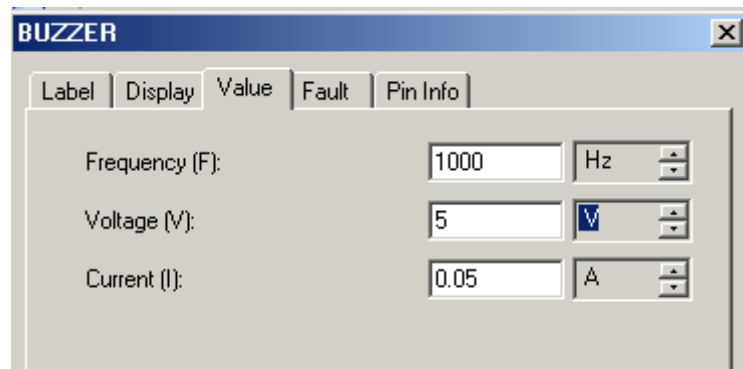




Circuit 6:

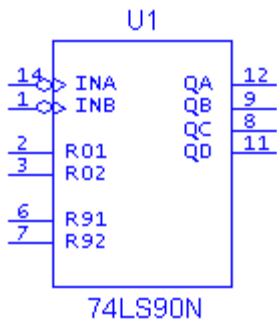


Select a Component

Database:	Component:	Symbol (ANSI)
Master Database	74LS69D	
	74LS69N	
	74LS73D	
	74LS73N	
	74LS74D	
	74LS74N	
	74LS75D	
	74LS75N	
	74LS76D	
	74LS76N	
	74LS77W	<p>Function:</p> <p>DECADE COUNTER</p>
	74LS78D	
	74LS78N	
	74LS83D	
	74LS83N	
	74LS85D	
	74LS85N	
	74LS86D	
	74LS86N	
	74LS90D	
	74LS90N	
	74LS91D	



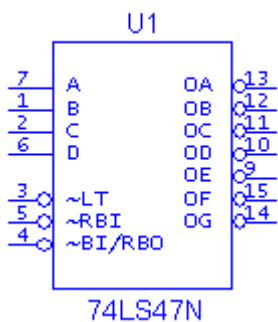


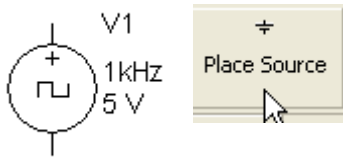Same as the 74LS90N except select 74LS47N.



Double click on symbol to set values on the device.

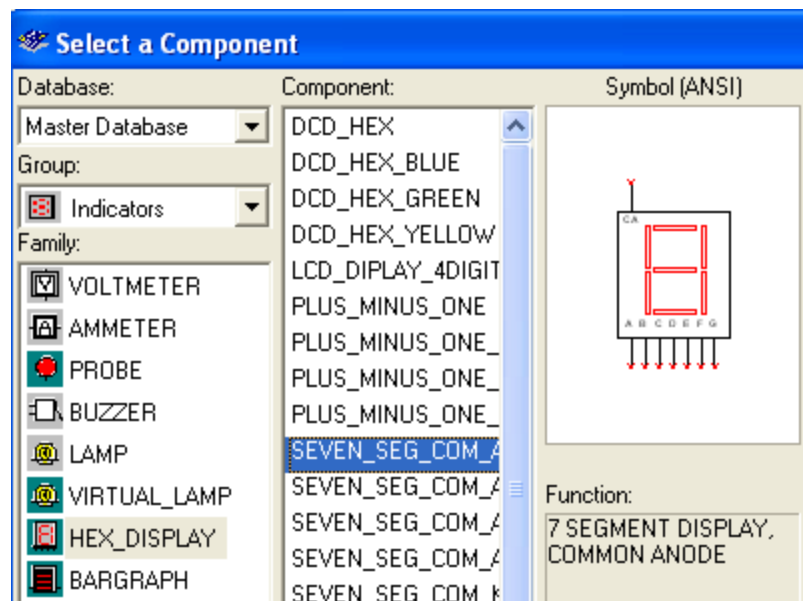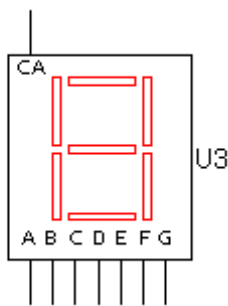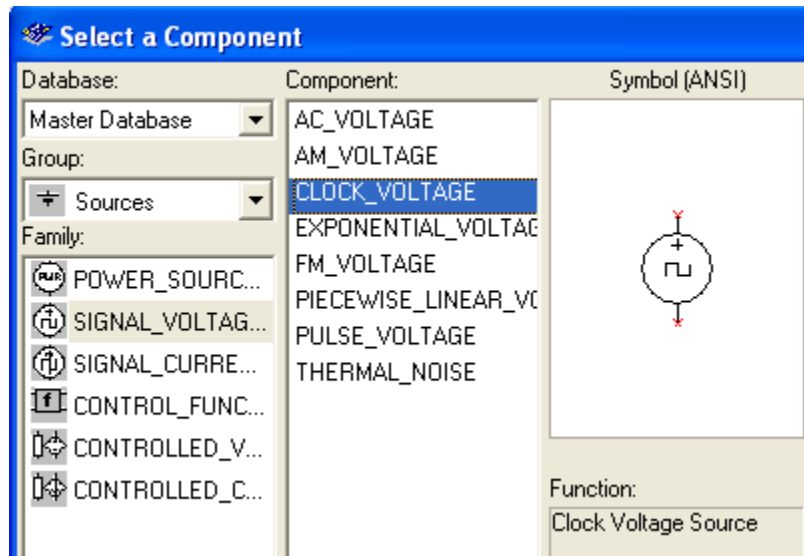
If the circuit is running when you change its speed, you will have to stop it and start it again for the new value to be recognized.





---

## Circuit 7:

Changing Page Size: Edit | Properties |

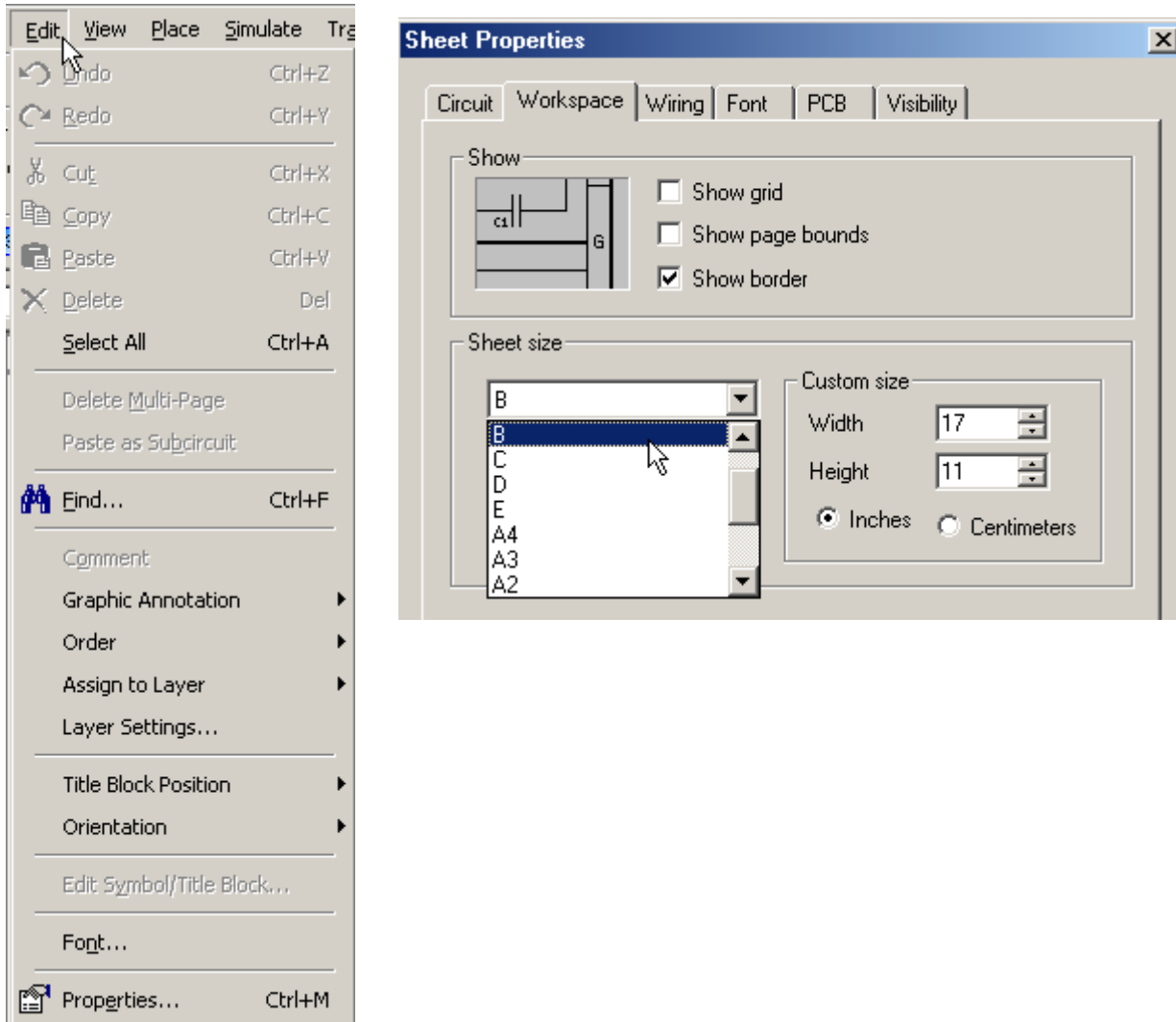

Circuit 8:

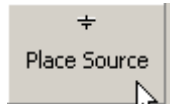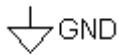


**Select a Component**

Database:	Component:	Symbol (ANSI)
Master Database	AC_POWER	
	DC_POWER	
	<b>DGND</b>	
	GROUND	
	NON_IDEAL_BATTERY	
	THREE_PHASE_DELTA	
	THREE_PHASE_WYE	
	VCC	
	VDD	
	VEE	
	VSS	

Database: Master Database  
 Group: Sources  
 Family: POWER\_SOURC..., SIGNAL\_VOLTAG..., SIGNAL\_CURRE..., CONTROL\_FUNC..., CONTROLLED\_V..., CONTROLLED\_C

Function:

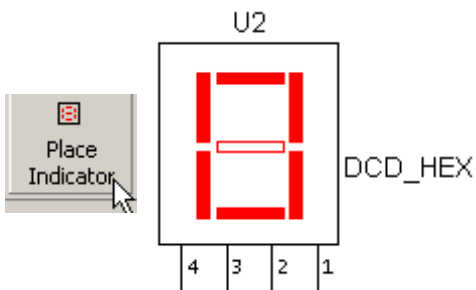


**Select a Component**

Database:	Component:	Symbol (ANSI)
Source Database	<b>DCD_HEX</b>	
	DCD_HEX_BLUE	
	DCD_HEX_GREEN	
	DCD_HEX_YELLOW	
	LCD_DIPLAY_4DIGIT	
	PLUS_MINUS_ONE	
	PLUS_MINUS_ONE_	
	PLUS_MINUS_ONE_	
	PLUS_MINUS_ONE_	
	PLUS_MINUS_ONE_	
	SEVEN_SEG_COM_A	
	SEVEN_SEG_COM_A	
	SEVEN_SEG_COM_A	
	SEVEN_SEG_COM_A	
	SEVEN_SEG_COM_A	


Database: Source Database  
 Group: Indicators  
 Family: VOLTMETER, AMMETER, PROBE, BUZZER, LAMP, VIRTUAL\_LAMP, HEX\_DISPLAY

Function:

## Naming a Wire

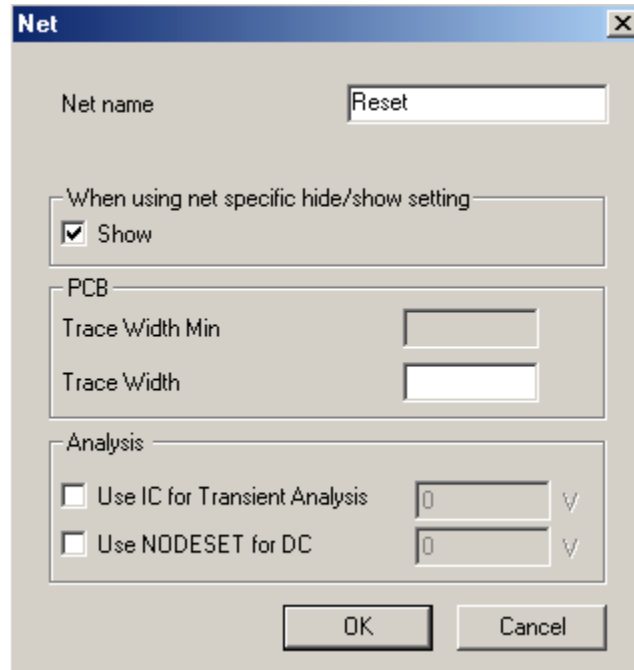


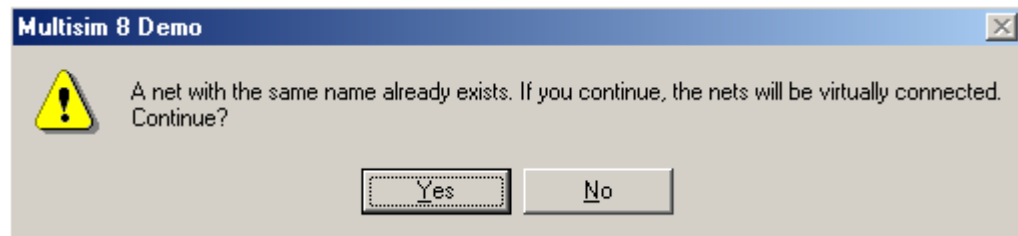A warning you get if you have previously used the same name.



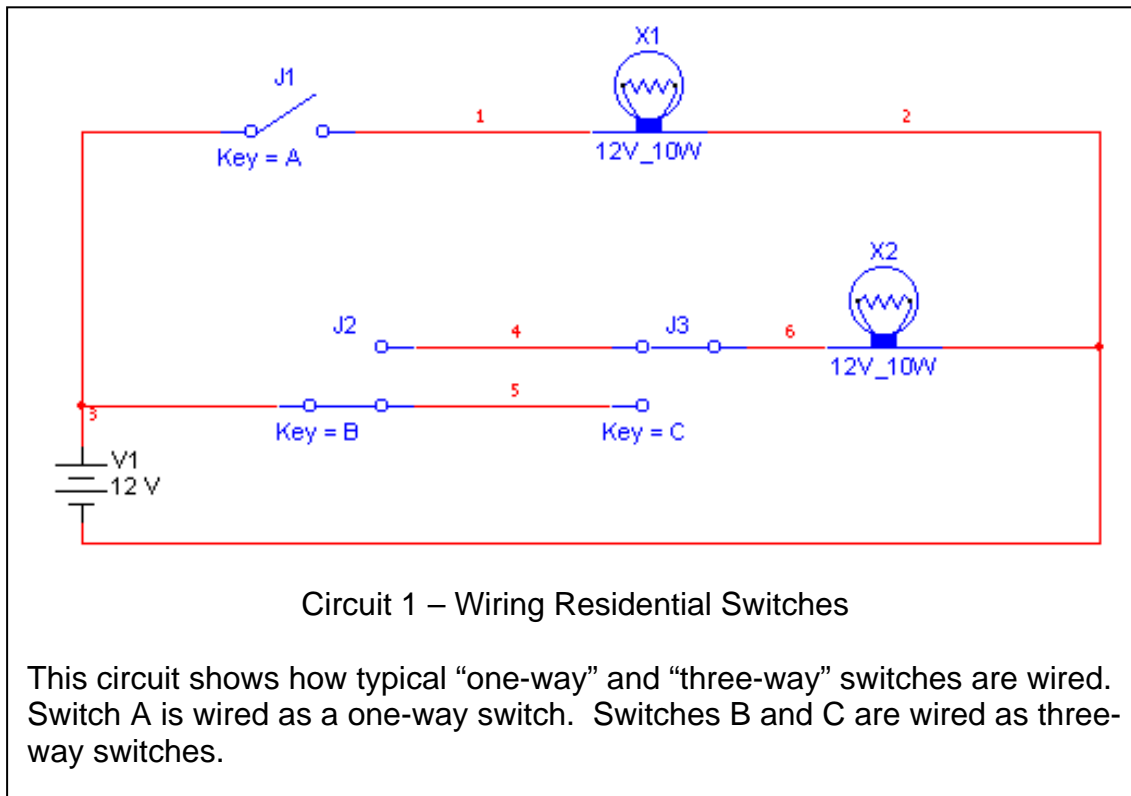
# Simulating Circuits

The circuits which we will construct and simulate are digital. In a digital circuit we are only concerned if a signal is present or not. A switch is an example of a digital circuit. It is either on or off. Terms used for the presence of a signal are **on**, **high**, **true**, and **one**. Terms used for the absence of a signal are **off**, **low**, **false** and **zero**. The following circuit shows how switches are wired in homes to make a one-way switch circuit and a three-way switch circuit.



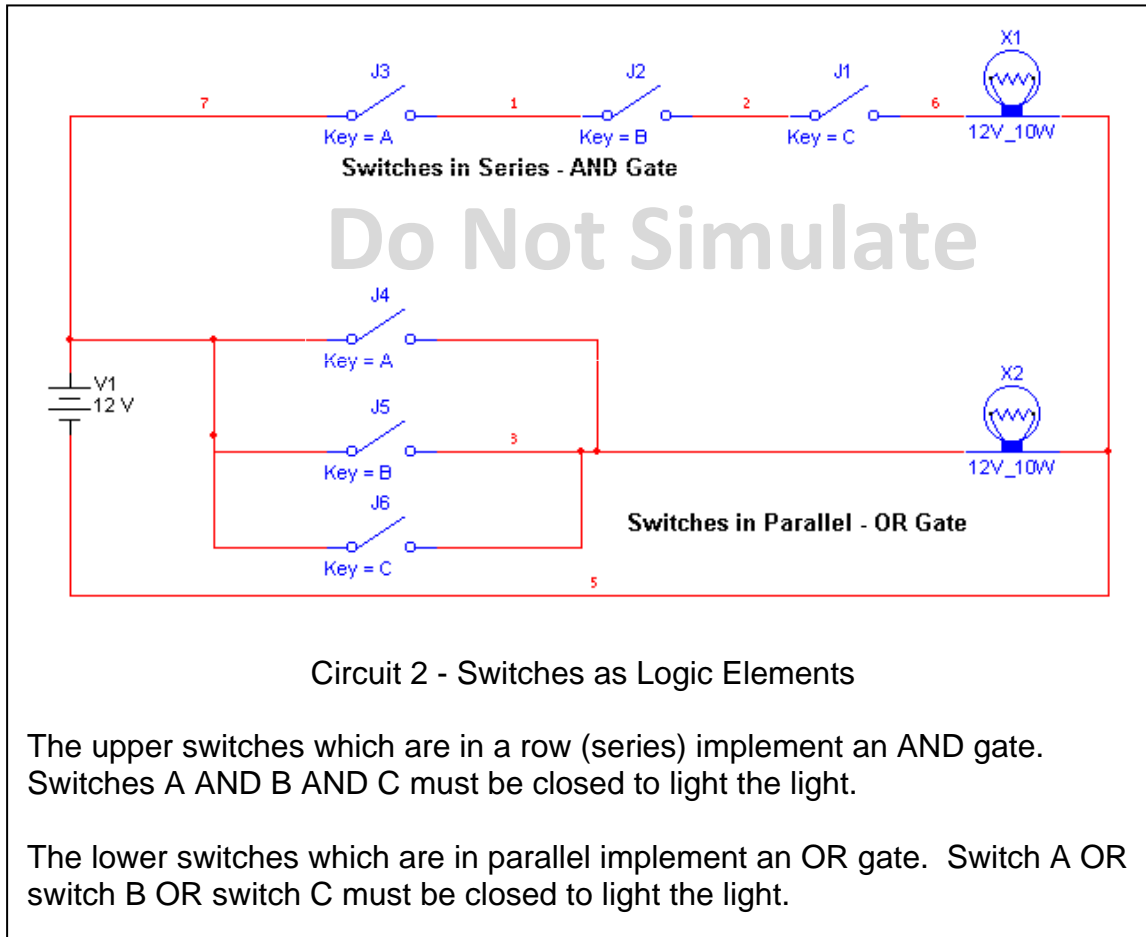Digital circuits are constructed so that they perform logic functions. The two most basic logic functions are the AND and OR. An AND circuit gives an output signal if all of its inputs (switches) are true (on). An OR circuit gives an output signal if at least one of its inputs is on. The following circuit shows how switches are wired to implement these functions.




**Do Not Simulate**


The following example shows how switches can be combined to make a “real” circuit. This implements a simple "Idiot Buzzer" system on an automobile.

The buzzer will sound if:

- the key is in the ignition AND the door is open
- OR the key is in the ignition AND the seat belts are not connected
- OR the lights are on AND the door is open.


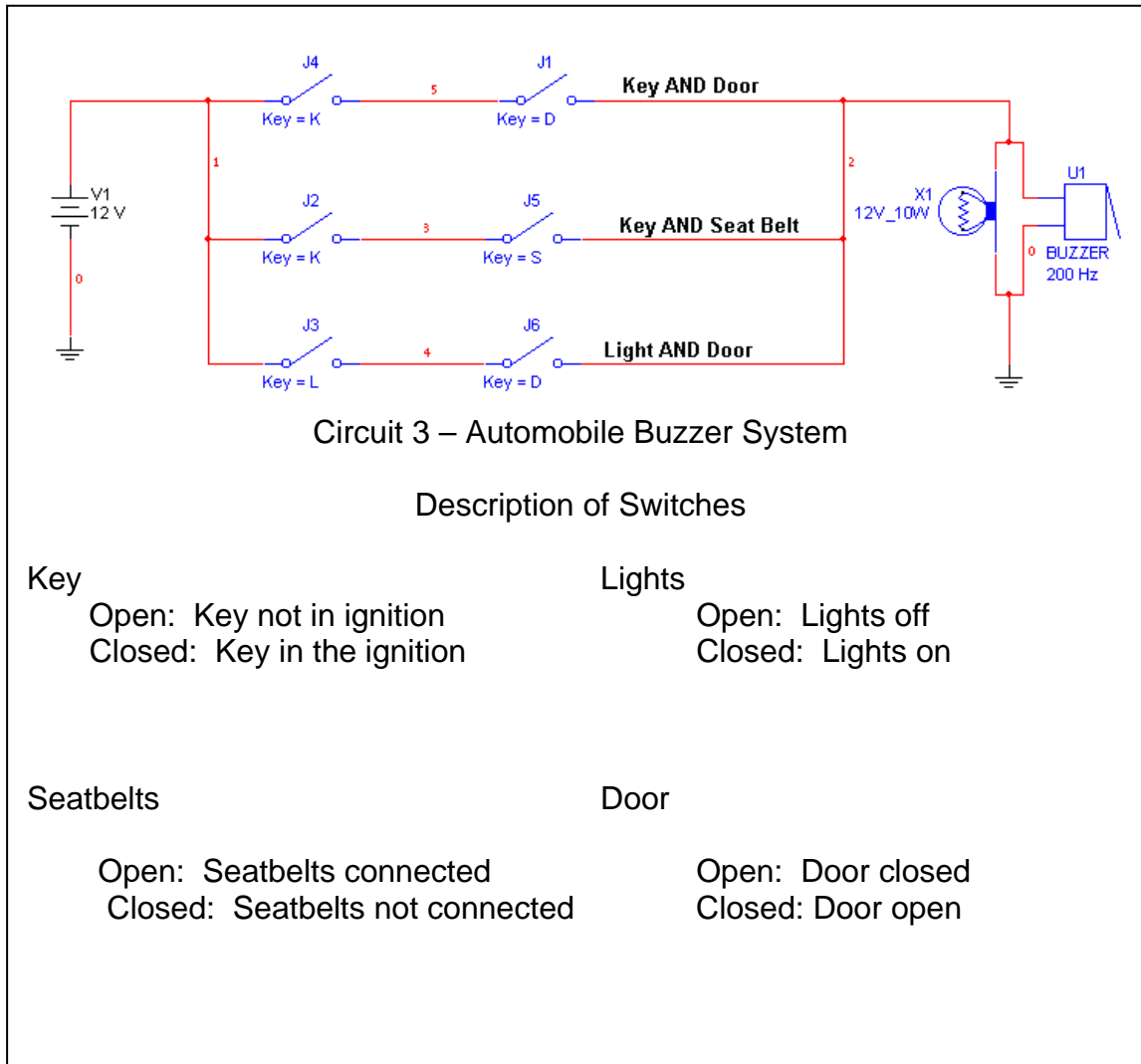
Note: A light is used in addition to the buzzer.



 
This circuit uses the ground Symbol .  All parts of the circuit which have the ground symbol are physically connected together even though the schematic does not show it.



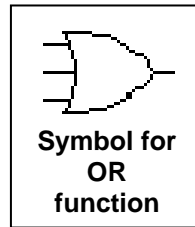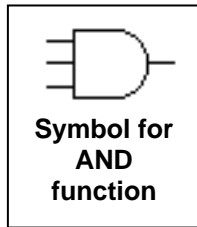There are symbols to represent the logic functions. The input signals are on the left and the output is on the right. These symbols show three signals ANDed and Ored but there could be any number of inputs. These symbols are normally used when the logic function is built using integrated circuits.



This circuit uses the integrated circuit symbols for the AND and OR logic gates.

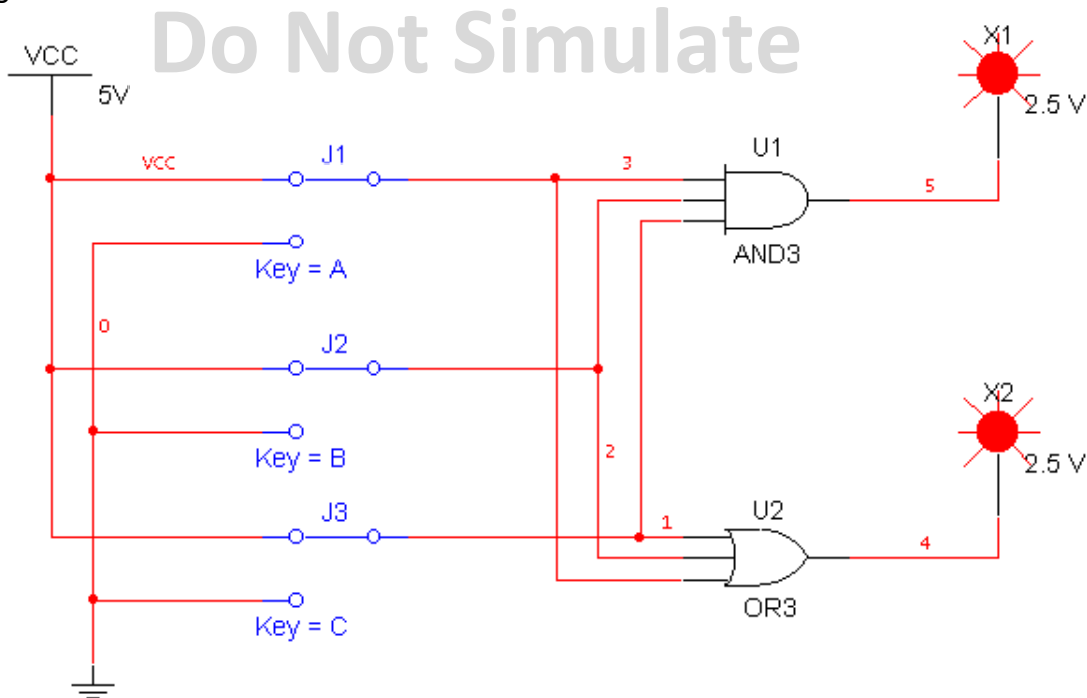


Circuit 4 – Integrated Circuit Logic Gates

Most integrated circuits use a 5 volt supply which is commonly referred to as

Vcc. The symbol  $\begin{matrix} +V_{cc} \\ | \end{matrix}$  represents the 5 volt battery. We also are using the

LED symbol  instead of a regular light.

This is how the integrated circuit form of the automobile idiot buzzer system would look.

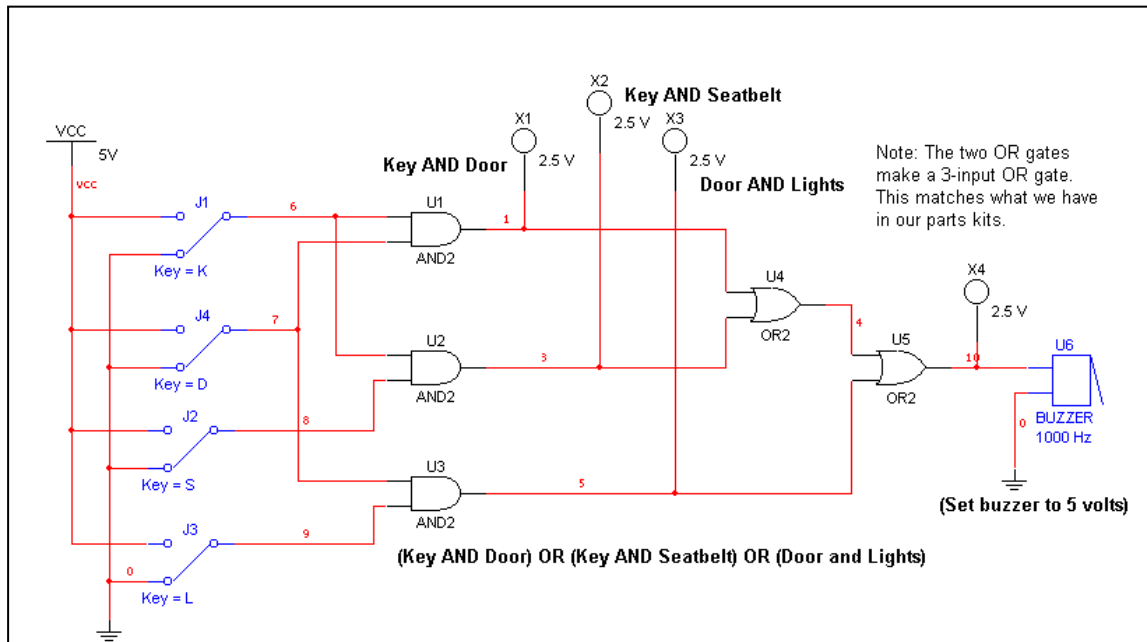

Circuit 5 – Integrated Circuit Form of Automobile Buzzer System

### Description of Switches

#### Key

Open: Key not in ignition  
 Closed: Key in the ignition

#### Lights

Open: Lights off  
 Closed: Lights on

#### Seatbelts

Open: Seatbelts connected  
 Closed: Seatbelts not connected

#### Door


Open: Door closed  
 Closed: Door open

## Decimal Numbers in Computers


Many applications require the use of a counter. The next circuit will count from 0 to 9 in binary. The binary number system uses base 2. Characters in the right column (sometimes labeled a) have the value  $2^0$ . In the next column to the left (labeled b) they have the value  $2^1$ . The next column (labeled c) is  $2^2$ . The next (d) is  $2^3$ . They evaluate from left to right as 8 - 4 - 2 - 1. The binary numbers from zero through 9 are:

For ease of use, we are using a modified binary system which only has values of zero through nine. This is referred to as binary coded decimal (BCD).


Binary				Decimal
d	c	b	a	
8	4	2	1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

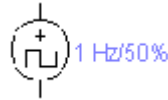

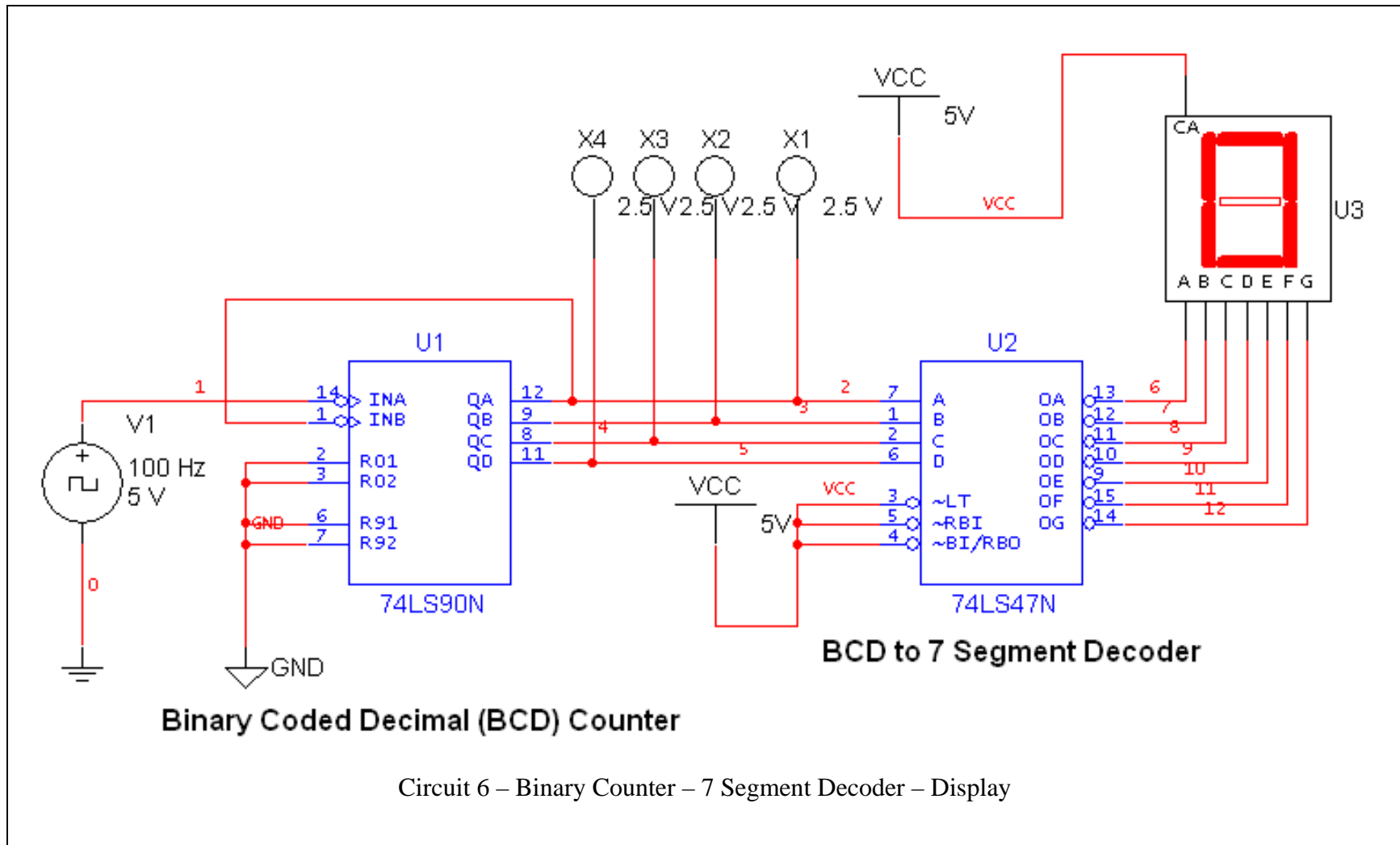
The next circuit consists of a signal generator set to give one transition per second. The counter integrated circuit, 7490, counts the transitions in binary and the value is shown on the four LED displays. The binary signals need to be converted to drive a 7 segment display. The binary to 7 segment decoder performs this task.



Next we will make a two decade counter which will count from 00 to 99. Change the size of the drawing sheet to size B. Move the circuit to the right side of the page by doing Edit | Select All (control A) and dragging the components to the desired position. Make a copy of the circuit by Select All and Paste (control V). Delete the signal generator on the left counter. The QD signal of the least significant digit will be used to clock the next stage. Place a wire from INA to QD.

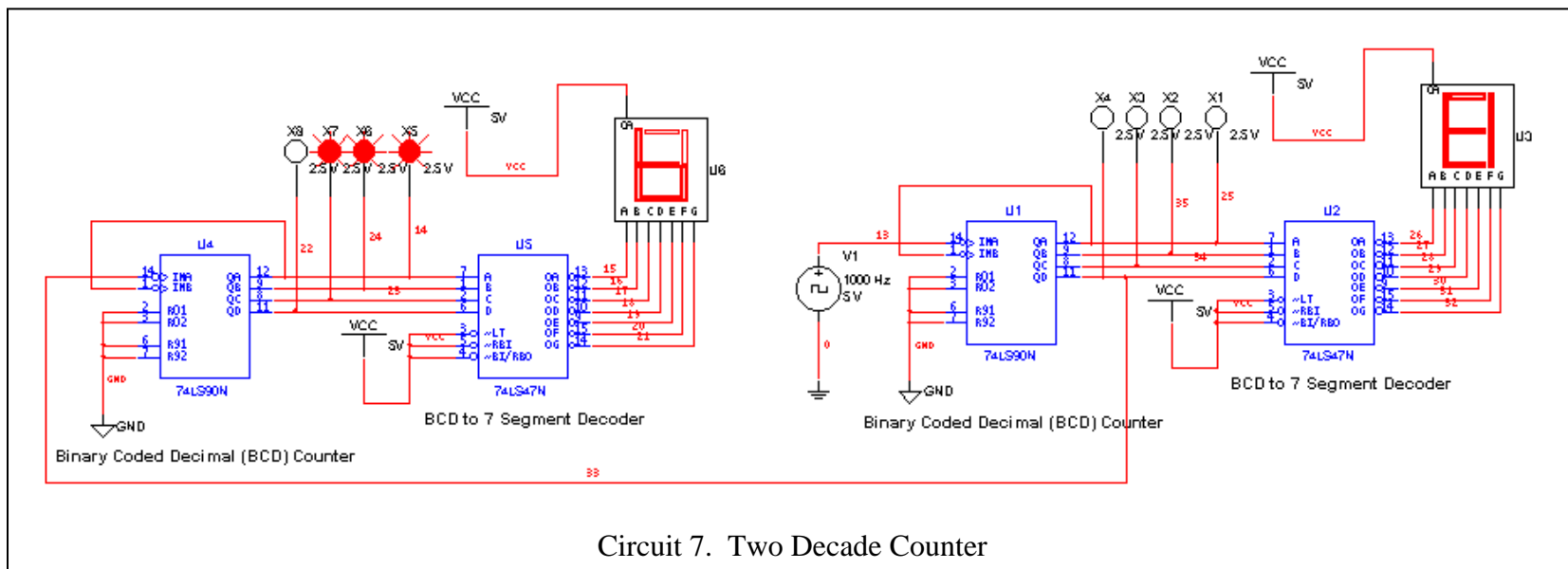


Create the following circuit. Use the DGND for the GND component. Use the DCD\_HEX component which combines the decoding and display in one component. This will speed simulation so the circuit will count faster. The switch will cause the counter to reset when connected to Vcc and to count normally when connected to ground. Double click on the wire connected to R01 and name the net Reset.

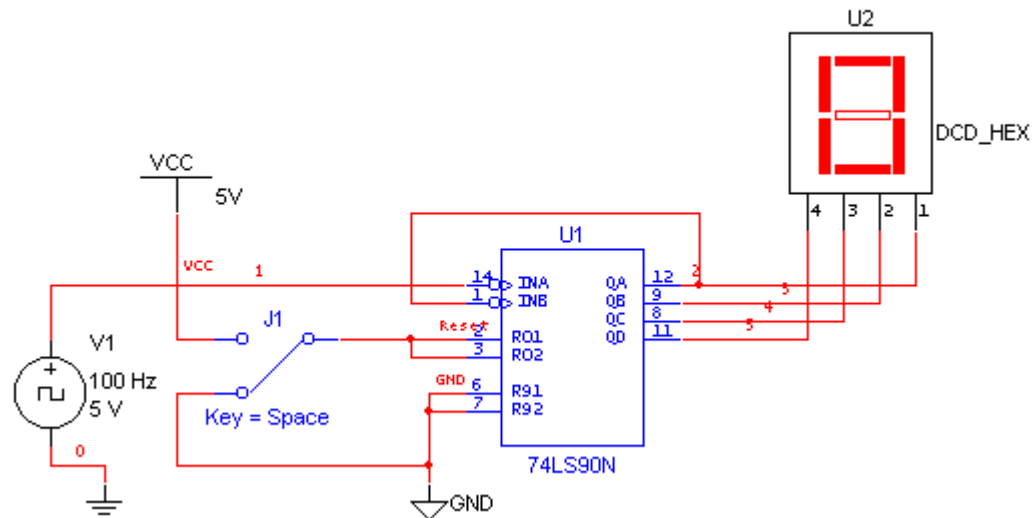

Circuit 8. Counter with Display

Copy the circuit three times to make a four digit counter. Double click the wire connected to R01 and name it Reset. You should get a warning that that name has been used. Click OK. This will make a connection between both wire named Reset without having to draw the line. Do the same to the other two counters. Connect the QD of a counter to the INA of the next counter. Set the clock frequency to 1000Hz. Remember to stop and then start the simulation after changing the clock speed.

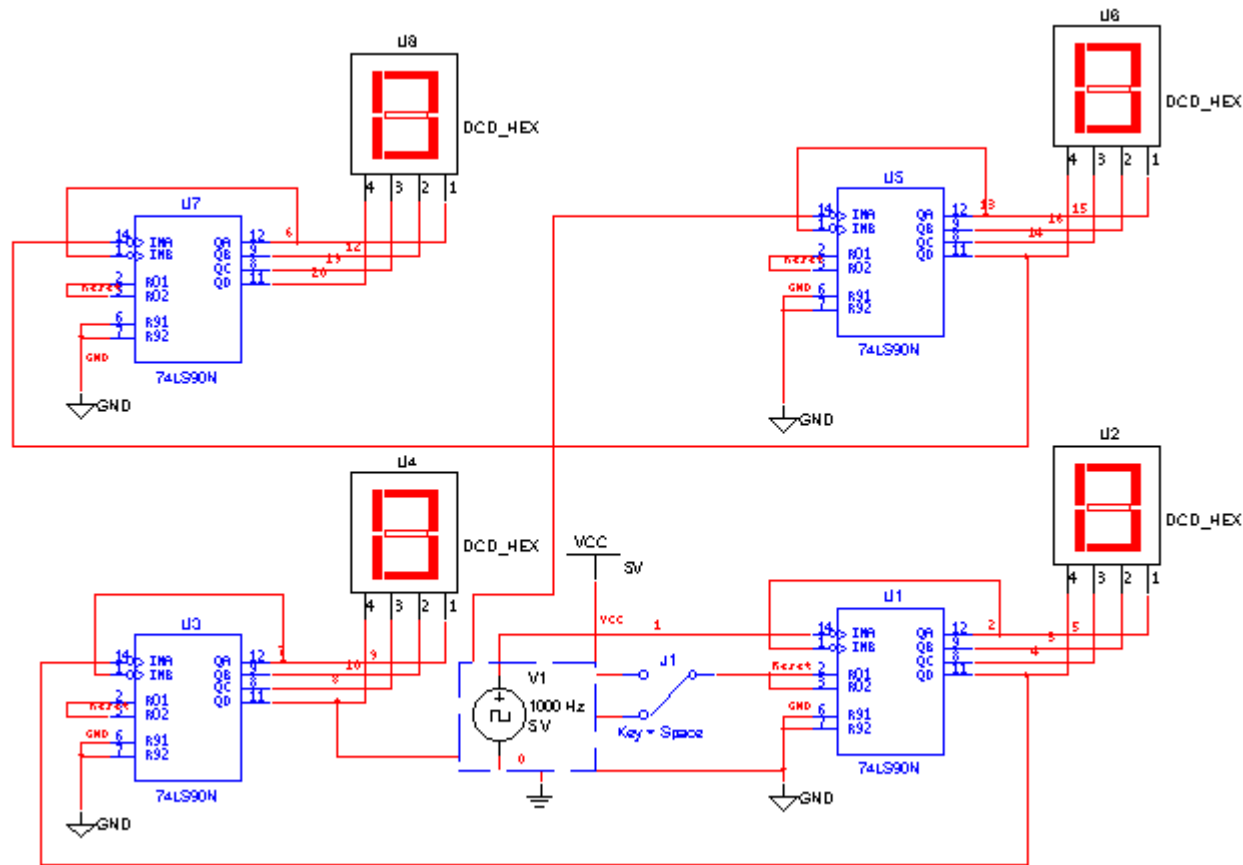

Circuit 9

## Hands-on Simulation:

In the time remaining before the break, you will construct and simulate some of the circuits discussed. You will do circuits in the following order. If you are running short of time, skip some of the first ones so you can finish circuits 3, 5, and 6. We will be building circuits 5 and 6 in the second portion of the module so it is helpful if you can finish and understand these two.

- **Circuit 1: Wiring Residential Switches**
- Circuit 2: Switches as Logic Elements** Do not simulate
- **Circuit 3: Automobile Buzzer System**
- Circuit 4: Integrated Circuit Logic Gates** Do not simulate
- **Circuit 5: Integrated Circuit Form of Automobile Buzzer System**
- **Circuit 6: Binary Counter – Seven Segment Decoder**
- Circuit 7: Two Digit Binary Counter – Seven Segment Decoder**
- Circuit 8: Simplified Binary Counter – Seven Segment Display**
- Circuit 9: Four Digit Binary Counter – Seven Segment Decoder**



## References:

### Simulation Software:

Electronics Workbench USA  
60 Industrial Park, #068  
Cheektowaga, NY 14227

[www.electronicworkbench.com](http://www.electronicworkbench.com)

### Electronic Components:

Jameco Electronic Components  
1355 Shoreway Road  
Belmont, CA 94002

[www.jameco.com](http://www.jameco.com)

### Breadboard:

PAD\_234 Digital/Analog Trainer

Electronix Express  
365 Blair Road  
Avene I, New Jersey 07001

[www.elexp.com/tst\\_234.htm](http://www.elexp.com/tst_234.htm)